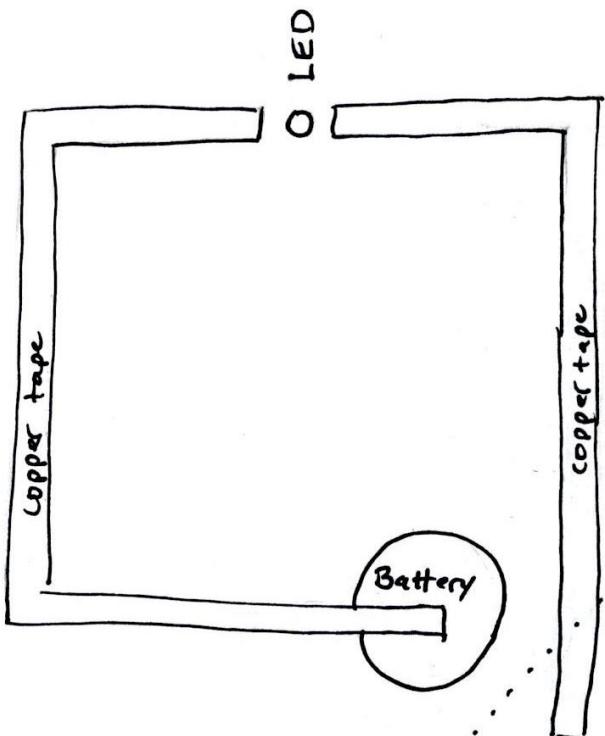


1. Peel the backing off one of your pieces of copper tape. Put it down in the lines as shown. If the tape is too long, cut it with scissors or carefully tear it. Fold the tape carefully at the corners.
2. Using the tip of a pair of scissors, make a small hole in the paper for the LED light to poke through.
3. Repeat with the second piece of copper tape.
4. See the circle that says LED? Carefully bend the 2 legs of the LED light so that it looks like it's doing the splits! Tape the legs on top of the copper tape, with the light in the middle over the circle.
5. Fold the corner of the card on the dotted line, and fold back again.
6. Place the coin battery in the circle that says "battery". Test your paper circuit by folding the corner and pressing the battery. If it doesn't light up, flip the battery over and try again.
7. Tape the battery in place but only cover about 1/3 of the battery's surface.
8. Enjoy your circuit!



1. Peel the backing off one of your pieces of copper tape. Put it down in the lines as shown. If the tape is too long, cut it with scissors or carefully tear it. Fold the tape carefully at the corners.
2. Repeat with the second piece of copper tape.
3. See the circle that says LED? Carefully bend the 2 legs of the LED light so that it looks like it's doing the splits! Tape the legs on top of the copper tape, with the light in the middle over the circle.
4. Fold the corner of the card on the dotted line, and fold back again.
5. Place the coin battery in the circle that says "battery". Test your paper circuit by folding the corner and pressing the battery. If it doesn't light up, flip the battery over and try again.
6. Tape the battery in place but only cover about 1/3 of the battery's surface.
7. Enjoy your circuit!

